

VLSI

September 22nd, 2026

Due date: September 29th, 2026

Name: _____ DU ID: _____ Section: _____

Lab 2 – Directions

Design a die that allows connecting the DAC from Lab 1 to the outside world.

Your lab report should document the following:

SCHEMATIC

- The schematic of the pad cell
- The schematic of the DAC
- The schematic of the padframe with the DAC. The padframe should be a square and you should design it to have the minimum number of required pad cells to connect all the DAC pinouts.
- All necessary explanations to support all the decisions taken during the design of the schematics.

LAYOUT

- The layout of the padframe with the DAC inside of it.
- All necessary explanations to support all the decisions taken during the design of the layout.

Good luck and have fun.